

2/EH—24 (ii) (Syllabus-2015)

2 0 1 8

( April )

PHYSICS

( Elective/Honours )

( Electromagnetism, Electronics—I )

[ PHY-02 (T) ]

Marks : 56

Time : 3 hours


*The figures in the margin indicate full marks  
for the questions*

Answer Question No. 1 and *any four* from the rest

1. (a) Find the electric potential on the surface of a nucleus having mass number 64, atomic number 30. Taking charge on proton to be  $1.6 \times 10^{-19}$  C and radius of proton  $1.2 \times 10^{-15}$  m. 3
- (b) A conductor of length 64 cm is bent into a square and a current of 4 A is passed through it. Find the magnetic field at the centre of the square. 3
- (c) A straight solenoid of length 1 m has 50 turns in the primary and 200 turns in the secondary. If the area of cross-section of the solenoid is  $4 \times 10^{-4}$  sq m, find its mutual inductance. 3

( 2 )

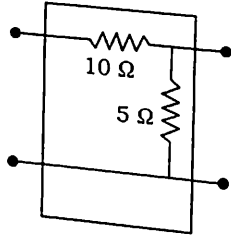- (d) Find the  $h$ -parameters of the circuit as shown in the figure below :



2. (a) State and prove Gauss' theorem in electrostatics and hence show that the total flux over a surface due to a charge lying outside is zero. 1+4+2=7
- (b) Obtain an expression for the potential due to a uniformly charged spherical shell at an external point. 4
3. (a) A point charge  $+q$  is placed at a distance  $d$  from the centre of an earthed conductor of radius  $R$ . Apply the method of electrical images to calculate the field on the sphere. 4
- (b) Derive an expression for Gauss' law in the presence of a dielectric. Also discuss the integral form of Gauss' law. 4+3=7
4. (a) An alternating e.m.f.  $E_0 \sin \omega t$  is applied to the ends of a circuit containing resistance  $R$ , self-inductance  $L$  and capacitance  $C$ . Calculate the impedance of the circuit, phase angle and the current at any instant. 4+1+2=7

8D/1709

( 3 )

- (b) What is the quality factor for an AC circuit? Prove that quality factor


$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad 1+3=4$$

5. (a) What do you mean by mutual inductance? On what factors does mutual induction depend? 2+2=4
- (b) State Faraday's law of electromagnetic induction. Prove that Faraday's law of electromagnetic induction can be expressed in the differential form

$$\vec{\nabla} \times \vec{E} = \frac{\partial \vec{B}}{\partial t}$$

and hence give the physical significance of the equation. 1+4+2=7

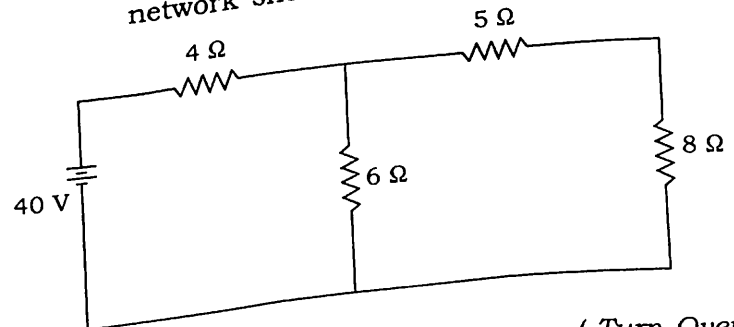6. (a) State and explain Thevenin's theorem. 1+5=6
- (b) Using Norton's theorem, find the current through the  $8 \Omega$  resistor in the network shown in the figure below : 5



( Turn Over )

8D/1709

7. (a) Describe with the help of a block diagram the working principle of a feedback amplifier. Derive an expression for the overall transfer gain. When does a feedback amplifier become oscillatory? 2+2+1=5

(b) What is a clipper circuit? Draw the circuit of a diode clipper which 'clips' the upper half of an input sin-wave lying above a reference voltage. 1+2=3

(c) Draw and describe in brief about a two-stage R-C coupled amplifier in CE mode. 3

8. (a) Write down the characteristics of an ideal Op-Amp. What are inverting and non-inverting terminals of an Op-Amp? Discuss the concept of virtual ground in Op-Amp. 3+2+2=7

(b) Show that OR, AND, NOR, NOT gates can be represented by using NAND gates only. 4

\*\*\*